

142544 – Nyabuto Lorna Njeri 4C
IoT Exe 2
PART A

CIRCUIT 1

1. $TR = 20 + 30 + 50 = 100\text{ohms}$
2. $TC = I = V/R = 125/100$
 $= 1.25\text{A}$
3. Current through each resistor
 $I_{20} = I_{30} = I_{50} = 1.25\text{ A}$
4. Voltage drop across each resistor
 $V=IR$
 $20\text{ohm} = 1.25 \times 20 = 25\text{V}$
 $30\text{ohm} = 1.25 \times 30 = 37.5\text{V}$
 $50\text{ohm} = 1.25 \times 30 = 62.5\text{V}$
5. Power dissipated
 $P = VI$
 $20\text{ohm resistor} = 25 \times 1.25 = 31.25\text{W}$
 $30\text{ohm resistor} = 37.5 \times 1.25 = 46.875\text{W}$
 $50\text{ohm resistor} = 62.5 \times 1.25 = 78.125\text{W}$

CIRCUIT 2

1. $TR = (1/100) + (1/50) = (1/100) + (2/100) = 3/100 =$
 33.33ohms
 $R_{\text{total}} = 20 + 33.33 = 53.33\text{ ohms}$
2. $TC = 125/53.33$
 $= 2.344\text{A}$
3. Current through each resistor
 $\text{Voltage} = 125 - (2.344 \times 20) = 125 - 46.875$
 $= 78.125\text{V}$

$$I_{100} = 78.125/100 \\ = 0.781\text{A}$$

$$I_{50} = 78.125/50 = 1.563\text{A}$$

4. Voltage drop on each resistor
 $20\text{ohm} = 2.344 \times 20 = 46.875\text{V}$

$$100\text{ohm} = 78.125\text{V}$$

$$50\text{ohm} = 78.125\text{V}$$

5. Power dissipated
 $20\text{ ohm} = 46.875 \times 2.344 \\ = 109.86\text{W}$
 $100\text{ ohm} = 78.125 \times 0.781 \\ = 61.03\text{W}$
 $50\text{ ohm} = 78.125 \times 1.563 \\ = 122.07\text{W}$